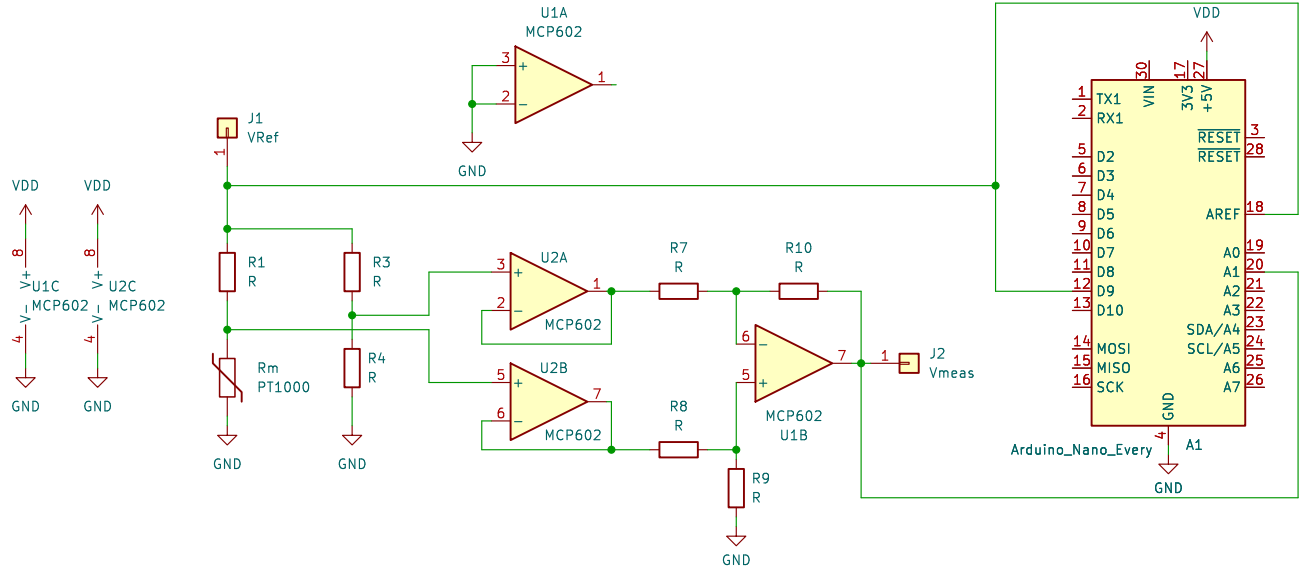


Thermometer with PT1000

Circuit



Dimensioning

Temperature measuring range should be from -20°C to 60°C . The resistance of the PT1000 is therefore in range $R_{\min} = 921.6\Omega$ to $R_{\max} = 1232.4\Omega$.

The bridge circuit R_1 , R_m , R_3 , R_4 should deliver approximately 0 V at minimum temperature. Thus R_4 should be R_{\min} . So R_4 is chosen $10\text{ k}\Omega \parallel 1\text{ k}\Omega = 0.909\text{ k}\Omega$, $R_1 = R_3 = 1\text{ k}\Omega$.

For the temperature measuring range and a reference voltage of $\approx 4.7\text{ V}$ the bridge output voltage is

$$V_a = V_{\text{ref}} \left(\frac{R_m}{R_1 + R_m} - \frac{R_4}{R_3 + R_4} \right) = 0.016\text{ V} \dots 0.356\text{ V}$$

The bridge output voltage is buffered by U_{2A} and U_{2B} and fed to a subtractor U_{1B} with a gain

$$v = \frac{R_{10}}{R_7} = \frac{R_9}{R_8} = 13$$

So $V_{\text{meas}} = v * V_a$ is in range $0.208\text{ V} \dots 4.635\text{ V}$.

V_{meas} is measured by an 10 bit ADC with the reference voltage V_{ref} .

Relationship of temperature and ADC value

In the temperature measuring range the value of PT1000 resistor could be approximated [1] by

$$R_m = R_0(1 + AT + BT^2)$$

with $R_0 = 1000 \Omega$, $A = 3.9083 \cdot 10^{-3} \frac{1}{^\circ\text{C}}$ and $B = -5.7750 \cdot 10^{-7} \frac{1}{^\circ\text{C}^2}$ within the accuracy of the ADC.

Vice versa the temperature could be calculated with

$$T_{1,2} = -\frac{A}{2B} \sqrt{\left(\frac{A}{2B}\right)^2 - \frac{1}{B} \left(1 - \frac{R_m}{R_0}\right)}$$

The value of PT1000 resistor is calculated

$$V_a = \frac{V_{\text{meas}}}{v} + V_{\text{ref}} \frac{R_4}{R_3 + R_4}$$

$$R_m = R_1 \frac{V_a}{V_{\text{ref}} - V_a}$$

The V_{meas} could be determined from ADC value D by

$$V_{\text{meas}} = \frac{DV_{\text{ref}}}{2^{10}}$$

Simplification

$$V_{\text{meas}} = D \frac{V_{\text{ref}}}{1024} \quad (1)$$

$$V_a = \frac{V_{\text{meas}}}{v} + kV_{\text{ref}} \quad \text{with} \quad k = \frac{R_4}{R_3 + R_4} \quad (2)$$

$$= D \frac{V_{\text{ref}}}{1024v} + kV_{\text{ref}} \quad (3)$$

$$R_m = R_1 \frac{V_a}{V_{\text{ref}} - V_a} \quad (4)$$

$$= R_1 \frac{D \frac{V_{\text{ref}}}{1024v} + kV_{\text{ref}}}{V_{\text{ref}} - \left(D \frac{V_{\text{ref}}}{1024v} + kV_{\text{ref}}\right)} = R_1 \frac{\frac{D}{1024v} + k}{1 - \left(\frac{D}{1024v} + k\right)} \quad (5)$$

$$= R_1 \frac{D + 1024vk}{1024v(1 - k) - D} \quad (6)$$

Note, the value of R_m does not depend on V_{ref} !

Measuring

The measurement of the temperature is done as follows

- drive the output D9, which actually supplies V_{ref} , to high
- wait 10 ms
- measure voltage
- drive the output to low
- wait 2 s to let the PT1000 cool down

References

- [1] Application Note, A Basic Guide to RTD Measurements.
<https://www.ti.com/lit/an/sbaa275a/sbaa275a.pdf>. Retrieved 2024-01-07